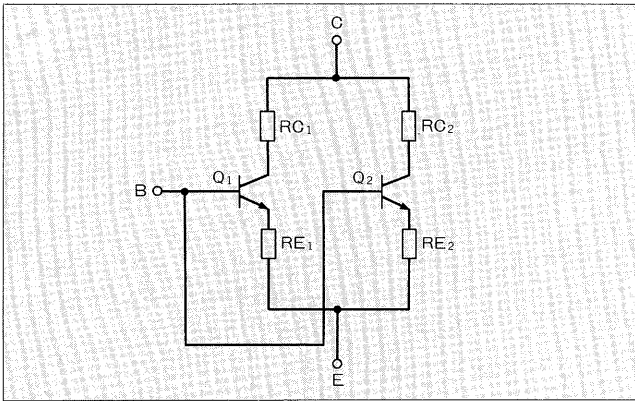


Fig. 2 Wiring resistances



collector wiring resistances are the same.

When the base drive wiring resistance is deviated, since an unbalance is produced in base current sharing, it has a large effect on sharing of the collector current.

2.2 Causes of current unbalance at turn-on and turn-off processes

2.2.1 Switching characteristic deviation

Deviation of the switching characteristic of a bipolar power transistor module produce a current unbalance when bipolar power transistor modules driven in parallel are switched. During the switching time, the storage time (t_{stg}) is the longest and the deviation width is also the widest, but when bipolar power transistor modules are driven in parallel, the base current conduction action described below has the effect of improving the deviation. Examples of the base voltage and current waveforms at turn-off are shown in Fig. 3. As shown in Fig. 3, as the turn-off action progresses, the base-emitter impedance increases and the base voltage (V_{BE}) changes in the negative direction.

The conduction action is shown in Fig. 4. The reverse bias base current of a device with a short storage time (t_{stg}) drops quickly and the reverse bias base current of a device with a long storage time (t_{stg}) increases. However, it must be noted that since the reverse bias base current is concentrated at the device with the longest storage time, RBSOA becomes narrow.

2.2.2 Wiring inductance deviation

The wiring inductances produce a current unbalance at switching as shown in Fig. 5.

Especially, the emitter wiring inductance is inserted into the base current path and has an affect on sharing of the base current.

The base inductance prevents conduction of the base current.

Therefore, for good current sharing, the wiring must be as short as possible and the emitter inductances, in particular, must be uniform.

Fig. 3 Example of operating waveforms at turn-off

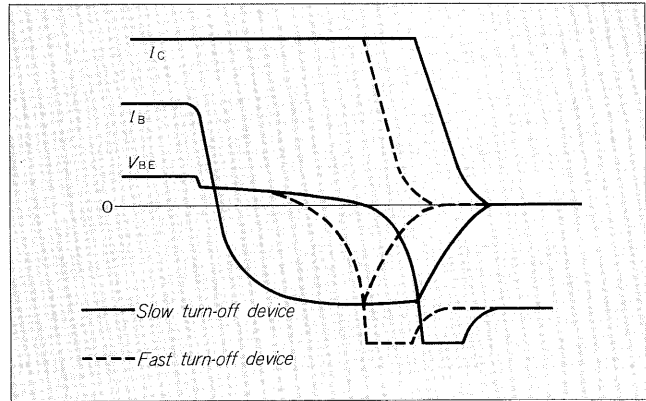


Fig. 4 Example of base current conduction action


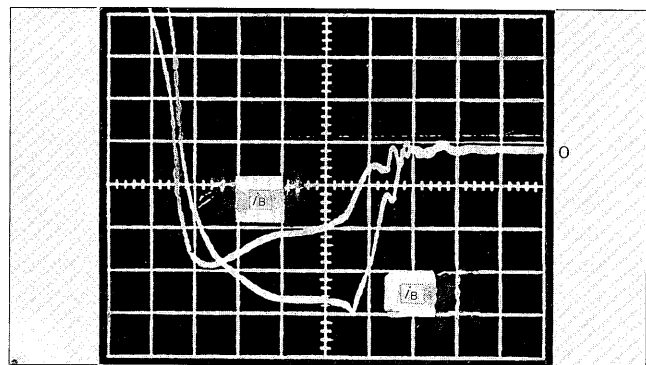


Fig. 5 Wiring inductances

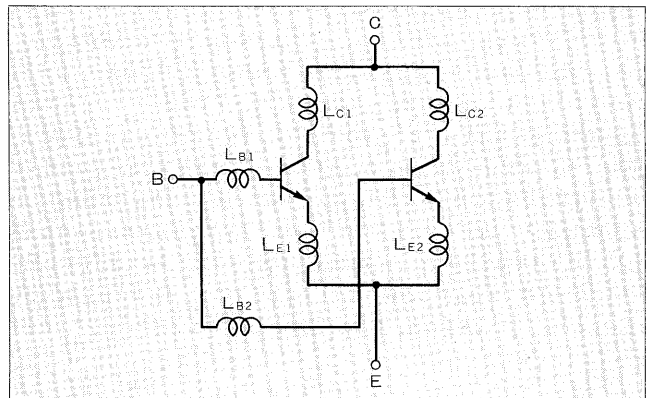


3. PARALLEL DRIVE METHOD

3.1 Wiring method

The ideal wiring method at parallel drive is said to be uniform and short. However, considering the wiring method at the product level it is difficult to satisfy this completely under various restriction.

Therefore, refinements which approach the ideal as close as possible are necessary. Especially, the main circuit

Fig. 6 Bipolar power transistor module parallel drive method

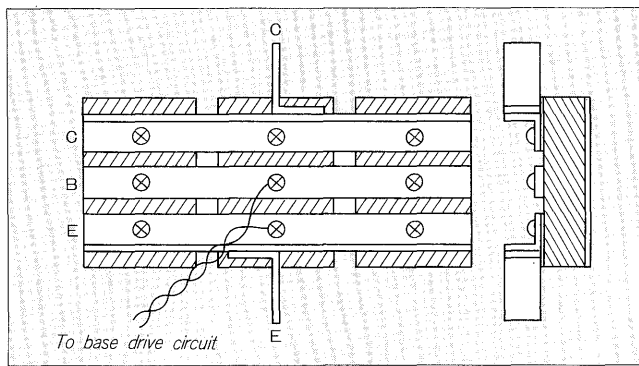

wiring structure is conclusive at parallel drive.


An example of the wiring structure of a parallel drive circuit using a bipolar power transistor module is shown in Fig. 6. The basic cautionary items are:

- (1) Arranging the power transistors as close together as possible so that the wiring between devices is short.
- (2) Using a structure and wire for the wiring between devices in which low and uniform inductances are considered. (Fig. 6 uses L angle.)
- (3) Extracting the collector and emitter wires from the center and avoiding wiring parallel to the base wiring. (Parallel wiring produces a current unbalance by magnetic coupling.)
- (4) Extracting the wires to the drive circuit from the center and twisting them tightly together.

3.2 Device characteristics management

The device characteristics that effect current sharing are h_{FE} , $V_{BE(sat)}$, $V_{CE(sat)}$, t_{on} , t_{stg} , and t_f . Managing the deviation of all these characteristics is almost impossible. In many cases, only one of these items is actually managed by using the fixed correlation between the direction and width of the deviation of these characteristics. Generally, h_{FE} is used to manage the characteristics of parallel drive devices, but since the management width of this deviation differs considerably with the drive conditions and wiring conditions, it must be selected by experimental certification by using devices with a different h_{FE} .

Fig. 7 Parallel drive of Darlington transistor with auxiliary base

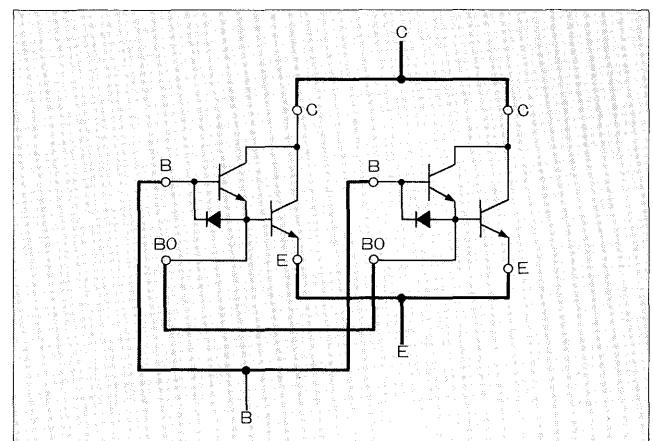

4. PARALLEL DRIVE BIPOLAR POWER TRANSISTOR MODULE

The mainstream of high capacity power transistors is the Darlington type. However, the deviation width of the characteristics of the Darlington transistor is larger than that of a single transistor.

Therefore, a Darlington transistor with auxiliary base terminal as shown in Fig. 7 was commercialized. Parallel drive as a single transistor at the preceding and following stages is possible by connecting them between the auxiliary bases.

5. CONCLUSION

The parallel drive techniques of bipolar power transistor modules were outlined above. Parallel drive techniques of bipolar power transistor modules will play an important role as the capacity of equipment which use power transistors is increased in the future.

The authors will be happy if this paper is of some assistance.