

Supplemental Explanation

Explanation 1 Arm

p. 175, 188

In switching circuits such as inverters, the parts that are made up of switches and diodes are called arms. As shown in Fig. 1, the circuit that supplies the load with an electric current from the power source is the upper arm. The circuit that draws electric current from the load to the power source is the lower arm.

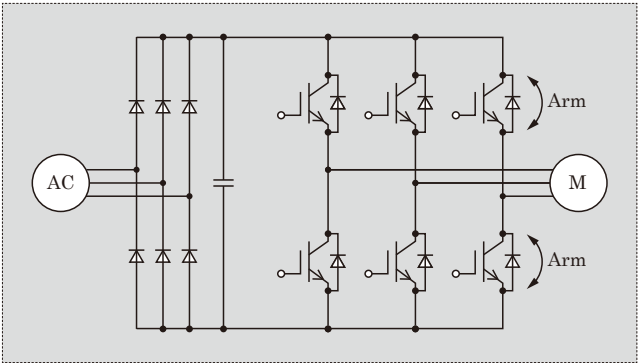


Fig.1 Switching circuit

Supplemental Explanation



* All brand names and product names in this journal might be trademarks or registered trademarks of their respective companies.